



UC Berkeley Teaching Professor Dan Garcia

Great Ideas in Computer Architecture (a.k.a. Machine Structures)

Combinational Logic Blocks



cs61c.org



UC Berkeley Professor Bora Nikolić



Doto Multiplexors





Data Multiplexor (here 2-to-1, n-bit-wide)



Combinational Logic Blocks (3)

"mux"





N instances of 1-bit-wide mux



ab S С 00 0 010 0 10 1 1 00 ()1 0110 ()Garcia, Nikolić \$0



 $\overline{s}a + sb$



Combinational Logic Blocks (5)

D







How many rows in the Truth Table?

abcd

0

10

11

when S=00, e=a when S=01, e=b when S=10, e=c when S=11, e=d

 $\zeta = S_1 S_0$

$e = \overline{s_1} \cdot \overline{s_0}a + \overline{s_1}s_0b + s_1\overline{s_0}c + s_1s_0d$



00

Combinational Logic Blocks (6)





Mux: is there any other way to do it?

Hint: NCAA tourney!



Ans: Hierarchically!

Combinational Logic Blocks (7)











Arithmetic Logic Unit (ALU)







Arithmetic and Logic Unit

- Most processors contain a special logic block called "Arithmetic and Logic Unit" (ALU)
- We'll show you an easy one that does ADD, SUB, bitwise AND (&), bitwise OR ()



when S=00, R=A+B when S=01, R=A-Bwhen S=10, R=A&B when S=11, R=A|B



Combinational Logic Blocks (9)











Combinational Logic Blocks (10)





Adder / Subtractor





Adder / Subtracter Design – how?

Truth-table, then determine canonical form, then minimize and implement as we've seen before

the problem down into that we can cascade or hierarchically layer



Combinational Logic Blocks (12)

Look at breaking smaller pieces







 $s_0 = a_0 \operatorname{XOR} b_0$ $c_1 = a_0 \operatorname{AND} b_0$



Combinational Logic Blocks (13)



 \mathbf{a}_0

0

0

1

1



Adder / Subtractor – One-bit adder (1/2)...

$$s_i = \operatorname{XOR}(a_i, b_i, c_i)$$
$$c_{i+1} = \operatorname{MAJ}(a_i, b_i, c_i) = a_i b_i$$



Combinational Logic Blocks (14)

 \mathbf{b}_i

0

0

0

0



$-a_ic_i + b_ic_i$



Adder / Subtractor – One-bit adder (2/2)...



$$s_i = \operatorname{XOR}(a_i, b_i, c_i)$$

+1 = MAJ $(a_i, b_i, c_i) = a_i b_i$



 C_{j}

Combinational Logic Blocks (15)



 $+a_ic_i + b_ic_i$





N 1-bit adders \rightarrow 1N-bit adder



What about overflow? Overflow = c_n ?

Combinational Logic Blocks (16)







Sum of two 2-bit numbers...





Combinational Logic Blocks (17)





Subtractor Design









Combinational Logic Blocks (19)



SUB

X	У	XOR(x,y)
0	0	0
0	1	1
1	0	1
1	1	0
		Garcia, Nikolić

BY NC SA



- Use muxes to select among input
 - S input bits selects 2^S inputs
 - Each input can be n-bits wide, indep of S
- Can implement muxes hierarchically
- ALU can be implemented using a mux
 - Coupled with basic block elements
- N-bit adder-subtractor done using N 1bit adders with XOR gates on input
 - XOR serves as conditional inverter





